

IT 2203

Combinational Logic



Dr. Md. Sazzadur Rahman

Professor

Institute of Information Technology
Jahangirnagar University, Savar, Dhaka.


Outlines

- Introduction
 - Motivation
 - Review of Boolean Algebra
 - Transformation of Logic Gates
- Specification
- Synthesis

Motivation: Combinational Logic

- Description
 - Language
 - Boolean algebra
 - Truth table
- Schematic Diagram
 - Inputs, Gates, Nets, Outputs
- Goal
 - Validity: correctness, turnaround time
 - Performance: power, timing, cost
 - Testability: yield, diagnosis, robustness

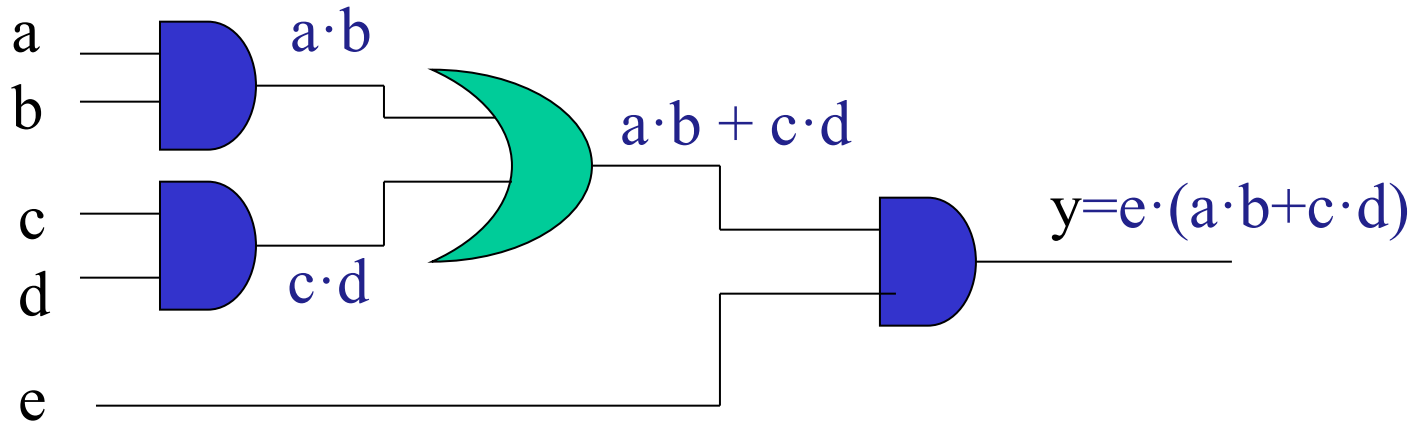Motivation: Combinational Logic vs. Boolean Algebra Expression



Schematic Diagram:

5 primary inputs, 1 primary output

4 components (gates)

9 signal nets

12 pins

Boolean Algebra:

5 literals

4 operators

Obj: min #terms
min #literals

Motivation: iClicker


Schematic Diagram:

5 primary inputs

4 components (gates)

9 signal nets

12 pins

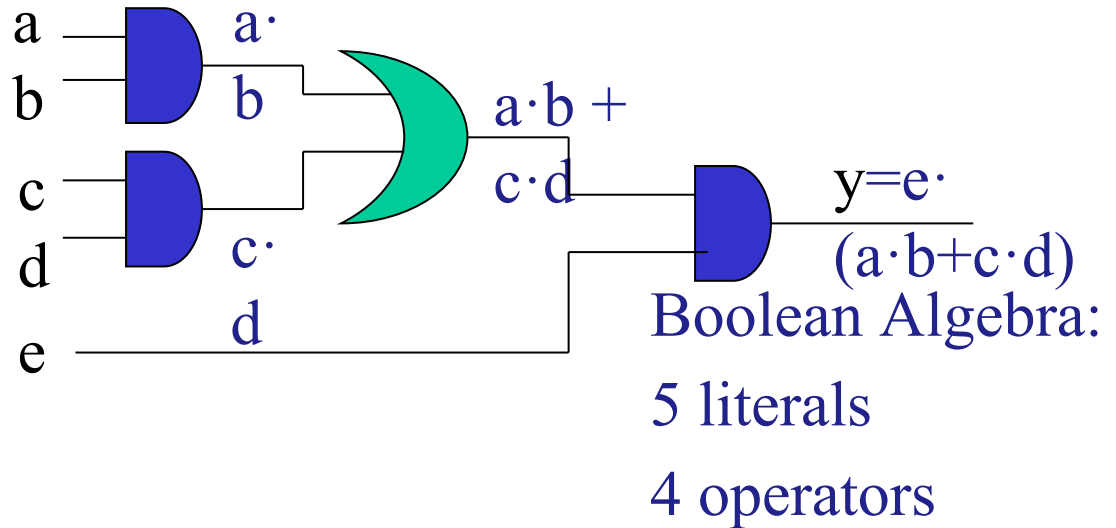

- A. #inputs
- B. #gates
- C. #nets
- D. #pins
- E. None

- I. #operators
- II. #literals + #operators
- III. #literals + 2 #operators

Schematic Diagram vs. Boolean Expression

- Boolean Expression: #literals, #operators
- Schematic Diagram: #gates, #nets, #pins
- One more example?

Some Definitions


- Complement: variable with a bar over it
 $\bar{A}, \bar{B}, \bar{C}$
- Literal: variable or its complement
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- Implicant: product of literals
 $ABC, A\bar{C}, BC$
- Minterm: product that includes all input variables
 $\bar{A}BC, A\bar{B}\bar{C}, ABC$
- Maxterm: sum that includes all input variables
 $(A+\bar{B}+C), (\bar{A}+B+\bar{C}), (A+\bar{B}+\bar{C})$

Digital Discipline: Binary Values

- Typically consider only two discrete values:
 - 1's and 0's
 - 1, TRUE, HIGH
 - 0, FALSE, LOW
- 1 and 0 can be represented by specific voltage levels, rotating gears, fluid levels, etc.
- Digital circuits usually depend on specific voltage levels to represent 1 and 0
- *Bit: Binary digit*

George Boole, 1815 - 1864

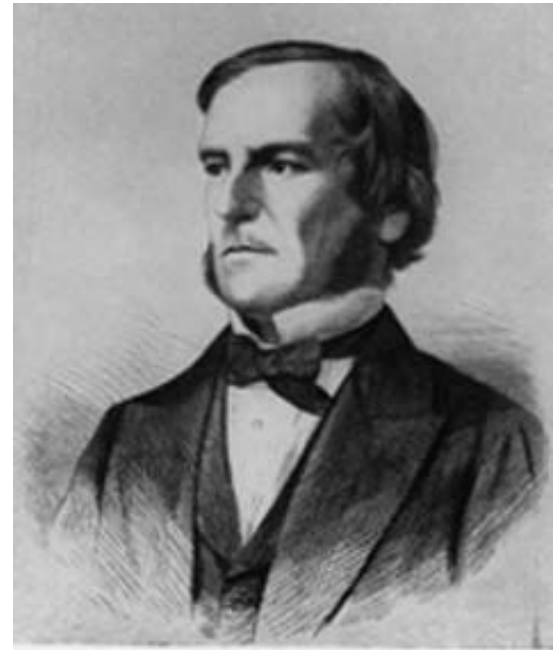- Born to working class parents
- Taught himself mathematics and joined the faculty of Queen's College in Ireland.
- Wrote *An Investigation of the Laws of Thought* (1854)
- Introduced binary variables
- Introduced the three fundamental logic operations: AND, OR, and NOT.



GEORGE BOOLE

Scanned at the American
Institute of Physics


Review of Boolean Algebra

Let B be a nonempty set with two binary operations, a unary operation $'$, and two distinct elements 0 and 1 . Then B is called a Boolean algebra if the following axioms hold.

- Commutative laws: $a+b=b+a$, $a \cdot b=b \cdot a$
- Distributive laws: $a+(b \cdot c)=(a+b) \cdot (a+c)$,
 $a \cdot (b+c)=a \cdot b+a \cdot c$
- Identity laws: $a+0=a$, $a \cdot 1=a$
- Complement laws: $a+a'=1$, $a \cdot a'=0$

Switching Algebra (A subset of Boolean Algebra)

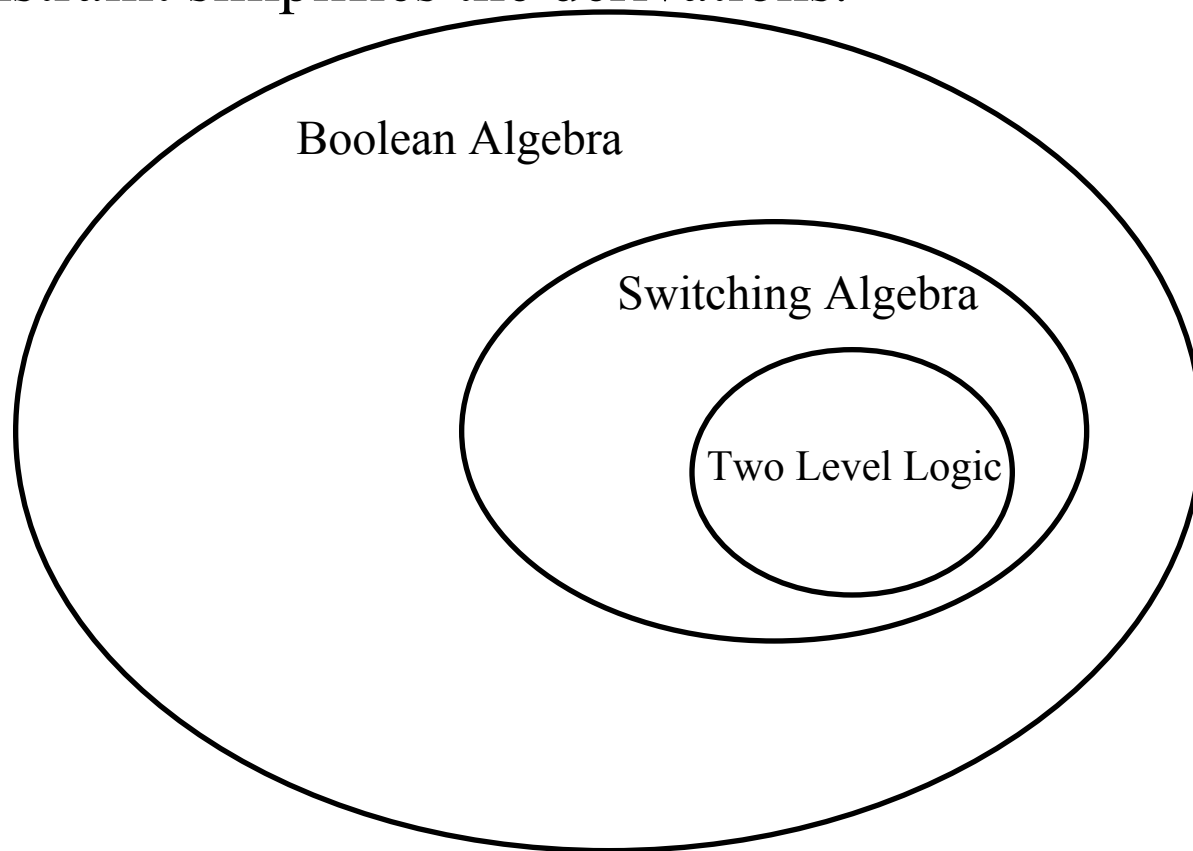- Boolean Algebra: Each variable may have multiple values.
- Switching Algebra: Each variable can be either 1 or 0. The constraint simplifies the derivations.



Switching Algebra


- Two Level Logic: Sum of products, or product of sums, e.g. $ab + a'c + a'b'$, $(a'+c)(a+b')(a+b+c')$
- Multiple Level Logic: Many layers of two level logic with some inverters, e.g. $((((a+bc)'+ab')+b'c+c'd)'bc+c'e$

Features of Digital Logic Design

- Multiple Outputs
- Don't care sets

Handy Tools:

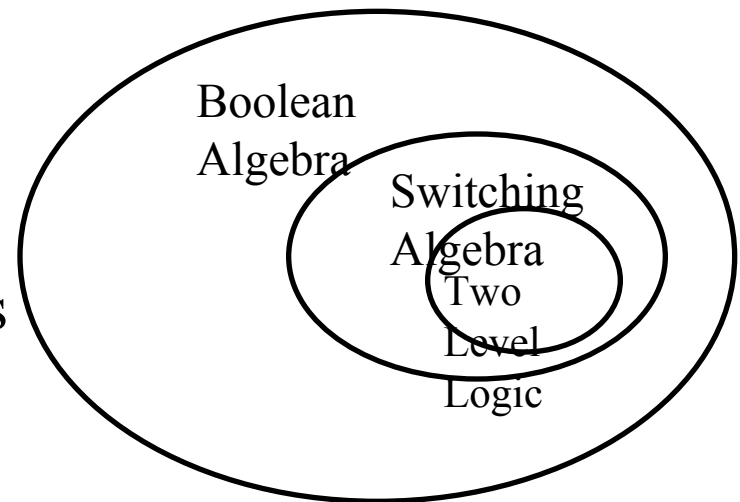- DeMorgan's Law: Complements
- Consensus Theorem
- Shannon's Expansion
- Truth Table
- Karnaugh Map (single output, two level logic)







Review of Boolean algebra and switching functions

AND, OR, NOT

AND		
Y	A B	
	0 0	0
	0 1	0
	1 0	0
	1 1	1

OR		
Y	A B	
	0 0	0
	0 1	1
	1 0	1
	1 1	1

NOT		
	A	Y
	0	1
	1	0

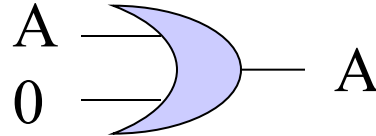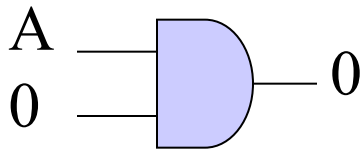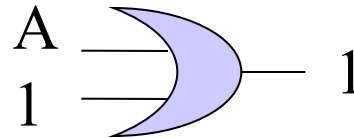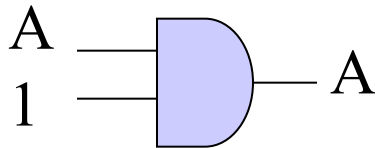

0 dominates in AND
0 blocks the output
1 passes signal A



1 dominates in OR
1 blocks the output
0 passes signal A

1. Identity $A * 1 = A$ $A + 1 = 1$
 $A * 0 = 0$ $A + 0 = A$



2. Complement $A + A' = 1$ $A * A' = 0$

T8. Distributive Law

$$A(B+C) = AB + AC$$

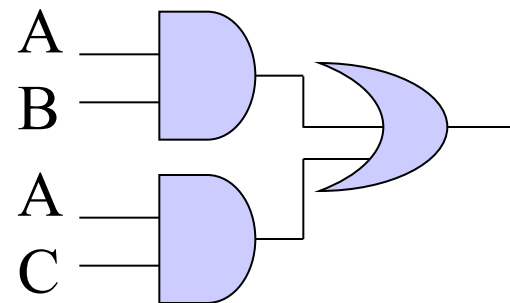
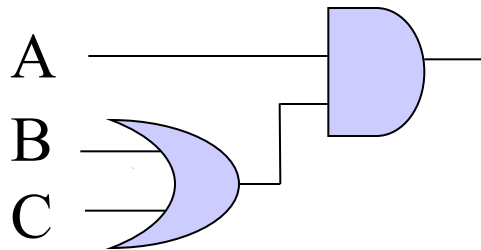


$$A+BC = (A+B)(A+C)$$

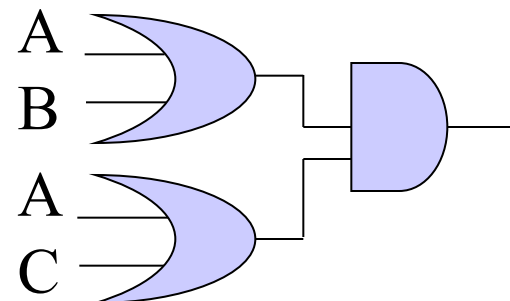
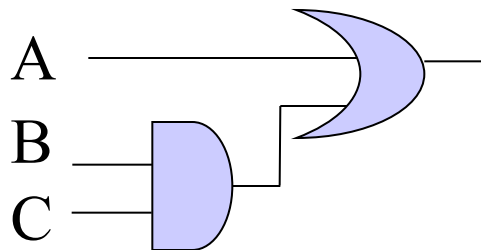


T7. Associativity

$$(A+B) + C = A + (B+C)$$

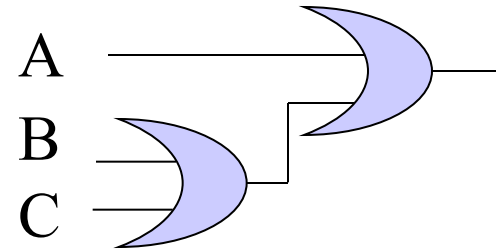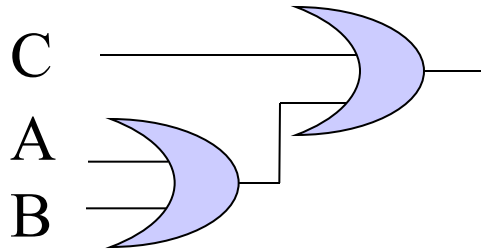

$$(AB)C = A(BC)$$

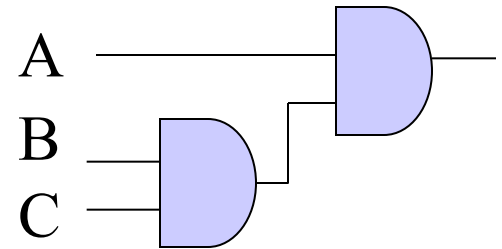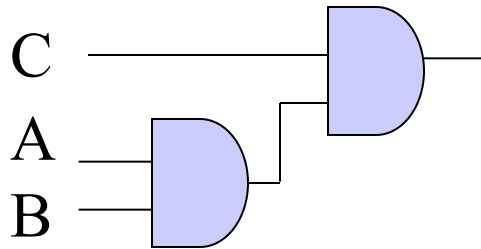

T12. DeMorgan's Law



$$(A+B)' = A'B' \quad (AB)' = A' + B'$$

T11. Consensus Theorem



$$AC + AB + BC' = AC + BC'$$

DeMorgan's Theorem

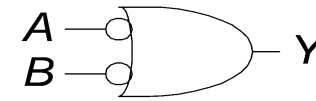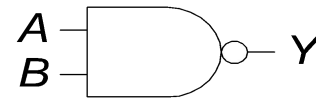- $Y = \overline{AB} = \overline{A} + \overline{B}$



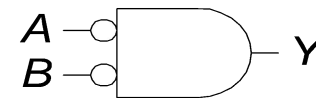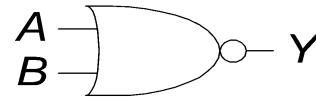- $Y = \overline{\overline{A} + \overline{B}} = \overline{A} \cdot \overline{B}$



Bubble Pushing

- Pushing bubbles backward (from the output) or forward (from the inputs) changes the body of the gate from AND to OR or vice versa.
- Pushing a bubble from the output back to the inputs puts bubbles on all gate inputs.



- Pushing bubbles on *all* gate inputs forward toward the output puts a bubble on the output and changes the gate body.



Consensus Theorem

- $AB + AC + B'C$
 $= AB + B'C$

- $(A+B)(A+C)(B'+C)$
 $= (A+B)(B'+C)$

Exercise: to prove the reduction using

- (1) Boolean algebra,
- (2) Logic simulation and
- (3) Shannon's expansion

Consensus Theorem: iClicker

Which term in $AB' + AC + BC$ can be deleted?

A. AB'

B. AC

C. BC

D. None of the above

Shannon's Expansion

- Shannon's expansion assumes a switching algebra system
- Divide a switching function into smaller functions
- Pick a variable x , partition the switching function into two cases: $x=0$ and $x=1$
 - $f(x)=xf(1)+x'f(0)$
 - $f(x,y)=xf(1,y)+x'f(0,y)$
 - $f(x,y,z,\dots)=xf(1,y,z,\dots)+x'f(0,y,z,\dots)$

Shannon's Expansion: iClicker

$$f(x,y,z)=xf(? ,y,z)+x'f(? ,y,z)$$

A. $?=0$

B. $?=1$.

$$f(x,y)=(x+f(? ,y))(x'+f(? ,y))$$

- A. $?=0$

- B. $?=1$.

Shannon's Expansion

Decompose the Switching function into minterms

$$\begin{aligned}f(x, y) &= xf(1, y) + x'f(0, y) \\&= x(yf(1,1) + y'(1,0)) + x'(yf(0,1) + y'f(0,0)) \\&= xyf(1,1) + xy'f(0,1) + x'yf(1,0) + x'y'f(0,0)\end{aligned}$$

Likewise, we can decompose the function into maxterms

$$\begin{aligned}f(x, y) &= (x + f(0, y))(x' + f(1, y)) \\&= (x + (y + f(0,0))(y' + f(0,1)))(x' + (y + f(1,0))(y' + f(1,1))) \\&= (x + y + f(0,0))(x + y' + f(0,1))(x' + y + f(1,0))(x' + y' + f(1,1))\end{aligned}$$

Switching Algebra

- Shannon's expansion and consensus theorem are used for logic optimization
- Shannon's expansion divides the problem into smaller functions
- Consensus theorem finds common terms when we merge small functions
- Karnaugh map mimics the above two operations in two dimensional space as visual aids.

Part I. Combinational Logic

I) Specification

- a. Language

- b. Truth Table

- c. Boolean Algebra

Canonical Expression: Sum of minterms and
Product of maxterms

- d. Incompletely Specified Function

Binary Addition

$$\begin{array}{r}
 5 \\
 + 7 \\
 \hline
 \end{array}$$


12 ← Sum
Carry

$$\begin{array}{rcccc}
 & 1 & 1 & 1 & \text{← Carry bits} \\
 & & 1 & 0 & 1 & \text{5} \\
 + & & 1 & 1 & 1 & \text{7} \\
 \hline
 & 1 & 1 & 0 & 0 & \text{12} \\
 \text{Carryout} & \swarrow & & \nwarrow & & \text{Sums}
 \end{array}$$

Binary Addition: Hardware

- Half Adder: Two inputs (a,b) and two outputs (carry, sum).
- Full Adder: Three inputs (a,b,c) and two outputs (carry, sum).

Half Adder

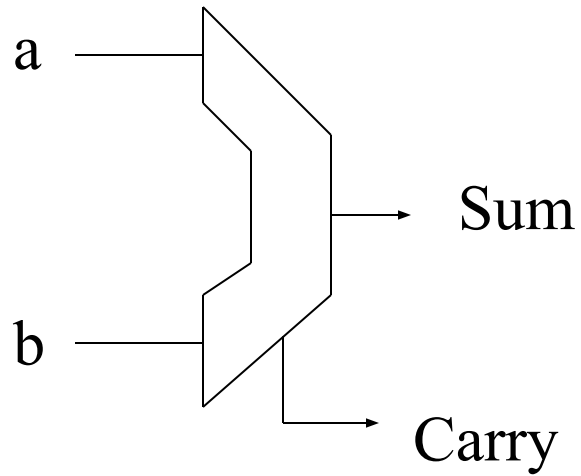

Truth Table

a	b	carry	sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Switching Function

Switching Expressions:

$$\text{Sum (a,b)} = a' \cdot b + a \cdot b'$$



$$\text{Carry (a, b)} = a \cdot b$$

Ex:

$$\text{Sum (0,0)} = 0' \cdot 0 + 0 \cdot 0' = 0 + 0 = 0$$


$$\text{Sum (0,1)} = 0' \cdot 1 + 0 \cdot 1' = 1 + 0 = 1$$
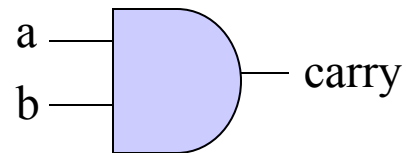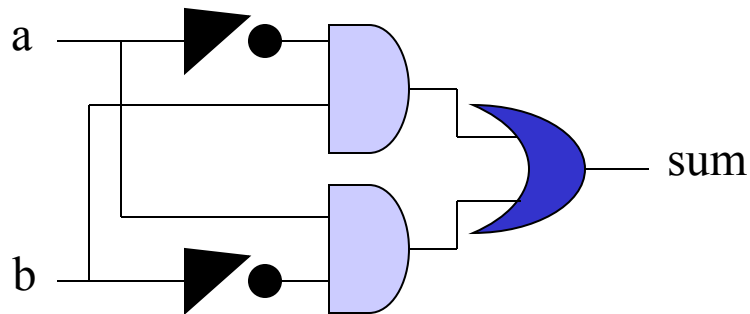
$$\text{Sum (1,1)} = 1' \cdot 1 + 1 \cdot 1' = 0 + 0 = 0$$



Full Adder

Truth Table

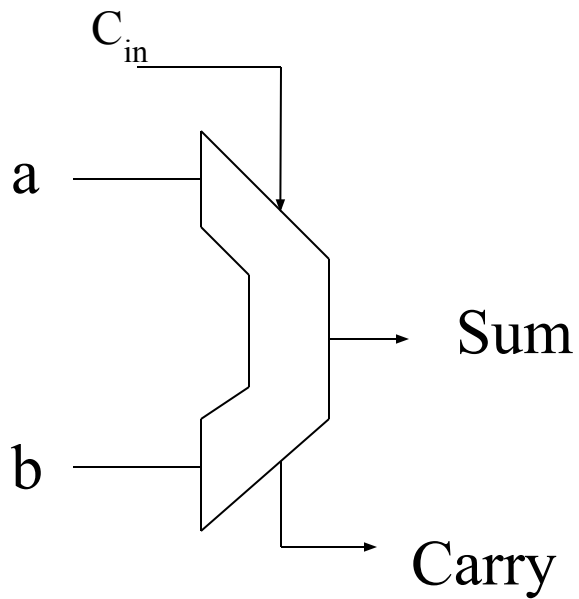

Id	a	b	c_{in}	carry	sum
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

Minterm and Maxterm

Id	a	b	c _{in}	carryout	
0	0	0	0	0	$a+b+c$
1	0	0	1	0	$a+b+c'$
2	0	1	0	0	$a+b'+c$
3	0	1	1	1	$a' b c$
4	1	0	0	0	$a'+b+c$
5	1	0	1	1	$a b' c$
6	1	1	0	1	$a b c'$
7	1	1	1	1	$a b c$

minterm

↑

maxterm

↖

Minterms

$$f_1(a,b,c) = a'bc + ab'c + abc' + abc$$

$$a'bc = 1 \text{ iff } (a,b,c) = (0,1,1)$$

$$ab'c = 1 \text{ iff } (a,b,c) = (1,0,1)$$

$$abc' = 1 \text{ iff } (a,b,c) = (1,1,0)$$

$$abc = 1 \text{ iff } (a,b,c) = (1,1,1)$$

$$f_1(a,b,c) = 1 \text{ iff } (a,b,c) = (0,1,1), (1,0,1), (1,1,0), \text{ or } (1,1,1)$$

$$\text{Ex: } f_1(1,0,1) = 1'01 + 10'1 + 101' + 101 = 1$$

$$f_1(1,0,0) = 1'00 + 10'0 + 100' + 100 = 0$$

Maxterms

$$f_2(a,b,c) = (a+b+c)(a+b+c')(a+b'+c)(a'+b+c)$$

$$a + b + c = 0 \text{ iff } (a,b,c) = (0,0,0)$$

$$a + b + c' = 0 \text{ iff } (a,b,c) = (0,0,1)$$

$$a + b' + c = 0 \text{ iff } (a,b,c) = (0,1,0)$$

$$a' + b + c = 0 \text{ iff } (a,b,c) = (1,0,0)$$

$$f_2(a,b,c) = 0 \text{ iff } (a,b,c) = (0,0,0), (0,0,1), (0,1,0), (1,0,0)$$

$$\begin{aligned} \text{Ex: } f_2(1,0,1) &= (1+0+1)(1+0+1')(1+0'+1)(1'+0+1) = 1 \\ f_2(0,1,0) &= (0+1+0)(0+1+0')(0+1'+0)(0'+1+0) = 0 \end{aligned}$$

$$f_1(a,b,c) = a'bc + ab'c + abc' + abc$$

$$f_2(a,b,c) = (a+b+c)(a+b+c')(a+b'+c)(a'+b+c)$$

$$f_1(a, b, c) = m_3 + m_5 + m_6 + m_7 = \Sigma m(3,5,6,7)$$

$$f_2(a, b, c) = M_0 M_1 M_2 M_4 = \Pi M(0, 1, 2, 4)$$

iClicker: Does $f_1 = f_2$?

A. Yes

B. No.

The coverage of a single minterm. E.g. $m_4 = ab'c'$

Id	a	b	c_{in}	carry	minterm $_4 = ab'c'$
0	0	0	0	0	0
1	0	0	1	0	0
2	0	1	0	0	0
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	0

Only one row has a 1.

The coverage of a single maxterm. E.g. $M_4 = a' + b + c$

Id	a	b	c _{in}	carry	maxterm ₄ = a+b+c
0	0	0	0	0	1
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	1
4	1	0	0	0	0
5	1	0	1	1	1
6	1	1	0	1	1
7	1	1	1	1	1

Only one row has a 0.

Incompletely Specified Function

Don't care set is important because it allows us to minimize the function

Id	a	b	f(a, b)
0	0	0	1
1	0	1	0
2	1	0	1
3	1	1	-

1) The input does not happen.

2) The input happens, but the output is ignored.

Examples:

- Decimal number 0... 9 uses 4 bits. (1,1,1,1) does not happen.
- Final carry out bit (output is ignored).

Incompletely Specified Function

Id	a	b	c	$g(a,b,c)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	-
3	0	1	1	1
4	1	0	0	1
5	1	0	1	-
6	1	1	0	0
7	1	1	1	1

$$\begin{aligned}
 g_1(a,b,c) &= a'b'c + a'bc + ab'b' + abc \\
 &= m_1 + m_3 + m_4 + m_7 \\
 &= \sum m(1,3,4,7)
 \end{aligned}$$

$$\begin{aligned}
 g_2(a,b,c) &= (a+b+c)(a'+b'+c) \\
 &= M_0 M_6 \\
 &= \prod M(0,6)
 \end{aligned}$$

iClicker: Does $g_1(a,b,c) = g_2(a,b,c)$?

A. Yes

B. No